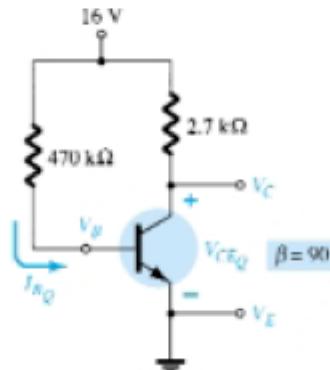


## Lista II – EN2602 Prof Marcelo Perotoni

1. For the fixed-bias configuration of Fig. 4.73, determine:

- (a)  $I_{BQ}$
- (b)  $I_{CQ}$
- (c)  $V_{CEQ}$
- (d)  $V_C$
- (e)  $V_B$
- (f)  $V_E$ .

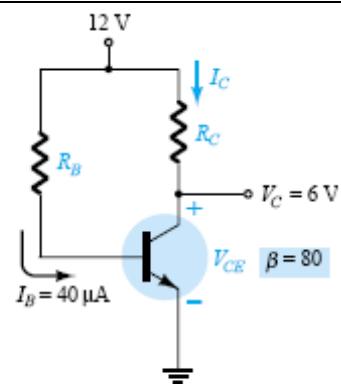


**Figure 4.73** Problems 1, 4, 11,  
47, 51, 52, 53

- (a)  $I_B=32.5\mu A$  (b)  $I_C=2.92mA$  (c)  $V_{CE}=8.11$  (d)  $V_C=8.11$  (e)  $V_B=0.725$  (f)  $V_E=0$

2. Given the information appearing in Fig. 4.74, determine:

- (a)  $I_C$ .
- (b)  $R_C$ .
- (c)  $R_B$ .
- (d)  $V_{CE}$ .



**Figure 4.74** Problem 2

- (a)  $I_C=3.2mA$  (b)  $R_C=1.875K$  (c)  $R_B=282.5K$  (d)  $V_{CE}=6V$

4. Find the saturation current ( $I_{C_{sat}}$ ) for the fixed-bias configuration of Fig. 4.73.

- (a)  $I_{C_{sat}}=5.92mA$

\* 5. Given the BJT transistor characteristics of Fig. 4.76:

- (a) Draw a load line on the characteristics determined by  $E = 21V$  and  $R_C = 3k\Omega$  for a fixed-bias configuration.
- (b) Choose an operating point midway between cutoff and saturation. Determine the value of  $R_B$  to establish the resulting operating point.
- (c) What are the resulting values of  $I_{CQ}$  and  $V_{CEQ}$ ?
- (d) What is the value of  $\beta$  at the operating point?
- (e) What is the value of  $\alpha$  defined by the operating point?
- (f) What is the saturation ( $I_{C_{sat}}$ ) current for the design?
- (g) Sketch the resulting fixed-bias configuration.
- (h) What is the dc power dissipated by the device at the operating point?
- (i) What is the power supplied by  $V_{CC}$ ?
- (j) Determine the power dissipated by the resistive elements by taking the difference between the results of parts (h) and (i).

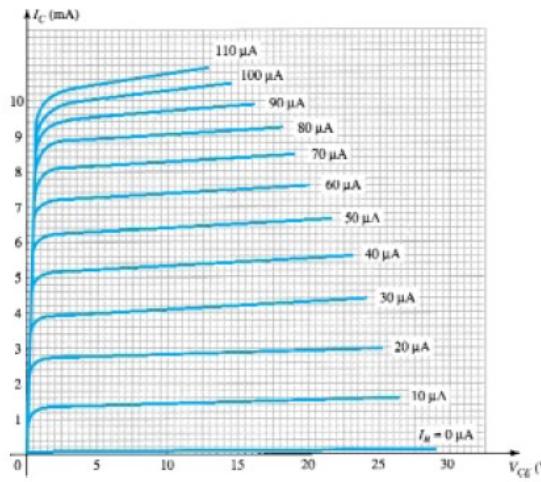


Figure 4.76 Problems 5, 10, 19, 35, 36

- (a) Reta com ponto de saturação 7mA e corte 21V (b) RB=812K considerando IB=25uA (c) IC=3.67mA (d)beta=146.8 (e) alfa=0.99 (f) ICsat=7mA (g) Rb=812K e Rc=3K (h) Ptrans=VCE.IC=36.7mW (i) VCC.IC=77mW (j) Presistores=Pfonte-Ptransistores=40mW

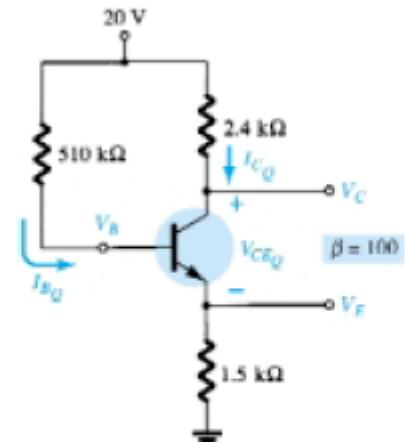


Figure 4.77 Problems 6, 9, 11, 20, 24, 48, 51, 54

6. For the emitter-stabilized bias circuit of Fig. 4.77, determine:

- (a)  $I_{BQ}$ .
- (b)  $I_{CQ}$ .
- (c)  $V_{CEQ}$ .
- (d)  $V_C$ .
- (e)  $V_B$ .
- (f)  $V_E$ .

- (a)  $IBQ=29.18\mu A$  (b)  $IcQ=2.42mA$  (c)  $VCEQ=8.61V$  (d)  $Vc=Vcc-IC.RC=1.3V$  (e)  $VB=VCC-IB.RB=5.12V$  (f)  $VE=4.39V$


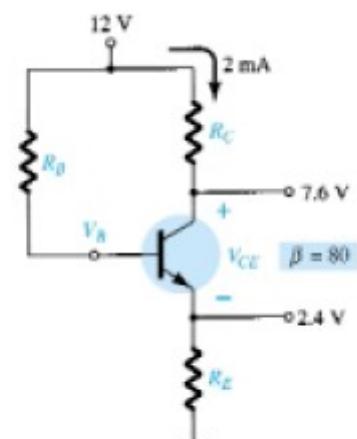


Figure 4.78 Problem 7

7. Given the information provided in Fig. 4.78, determine:

- (a)  $R_C$ .
- (b)  $R_E$ .
- (c)  $R_B$ .
- (d)  $V_{CE}$ .
- (e)  $V_B$ .

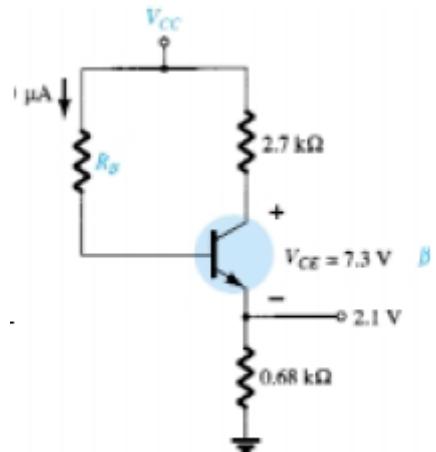- (a)  $RC=2K2$  (b)  $RE=1K2$  (c)  $IB=25\mu A$  (d)  $VCE=5.2$  (e)  $VB=3.1$



8. Given the information provided in Fig. 4.79, determine:

- (a)  $\beta$ .
- (b)  $V_{CC}$ .
- (c)  $R_B$ .


Figure 4.79 Problem 8

**Observação – corrente na base = 20uA (foi cortada na figura)**

- (a) Beta=154.5 (b) VCC=17.5 (c) RB=735K

9. Determine the saturation current ( $I_{C_{sat}}$ ) for the network of Fig. 4.77.

$$I_{C_{sat}} = 5.12 \text{ mA}$$

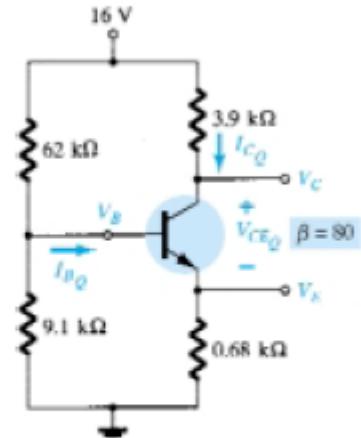


12. For the voltage-divider bias configuration of Fig. 4.80, determine:

- (a)  $I_{B_Q}$ .
- (b)  $I_{C_Q}$ .
- (c)  $V_{CEQ}$ .
- (d)  $V_C$ .
- (e)  $V_E$ .
- (f)  $V_B$ .

Figure 4.80 Problems 12, 15, 18, 20, 24, 49, 51, 52, 55

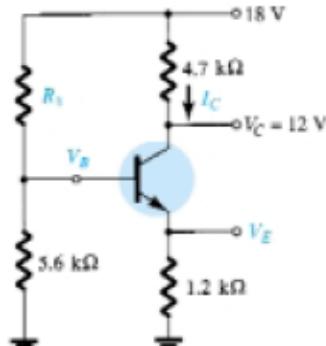- (a)  $I_B = 21.5 \mu\text{A}$  (b)  $I_{CQ} = 1.71 \text{ mA}$  (c)  $V_{CEQ} = 8.16 \text{ V}$  (d)  $V_C = 9.32 \text{ V}$  (e)  $V_E = 1.16 \text{ V}$  (f)  $V_B = 1.86 \text{ V}$



13. Given the information provided in Fig. 4.81, determine:

- (a)  $I_C$ .
- (b)  $V_E$ .
- (c)  $V_B$ .
- (d)  $R_1$ .

Figure 4.81 Problem 13

**Observação –  $R_2 = 5\text{K}6$  (figura com definição deficiente)**

- (a)  $I_C = 1.27 \text{ mA}$  (b)  $V_E = 1.52 \text{ V}$  (c)  $V_B = 2.22 \text{ V}$  (d)  $R_1 = 39\text{K}8$

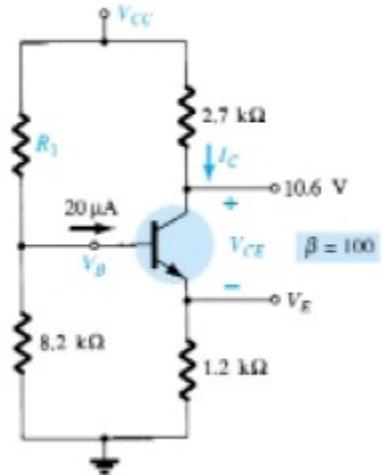


Figure 4.82 Problem 14

14. Given the information appearing in Fig. 4.82, determine:

- (a)  $I_C$ .
- (b)  $V_E$ .
- (c)  $V_{CC}$ .
- (d)  $V_{CE}$ .
- (e)  $V_B$ .
- (f)  $R_1$ .

(a)  $I_C=2\text{mA}$  (b)  $V_E=2.4\text{V}$  (c)  $V_{CC}=16\text{V}$  (d)  $V_{CE}=8.2\text{V}$  (e)  $V_B=3.1$  (f)  $R_1=32\text{k}\Omega$

15. Determine the saturation current ( $I_{C_{sat}}$ ) for the network of Fig. 4.80.

$$I_{C_{sat}}=3.49\text{mA}$$

\* 16. Determine the following for the voltage-divider configuration of Fig. 4.83 using the approximate approach if the condition established by Eq. (4.33) is satisfied.

- (a)  $I_C$ .
- (b)  $V_{CE}$ .
- (c)  $I_B$ .
- (d)  $V_E$ .
- (e)  $V_B$ .

\* 17. Repeat Problem 16 using the exact (Thévenin) approach and compare solutions. Based on the results, is the approximate approach a valid analysis technique if Eq. (4.33) is satisfied?


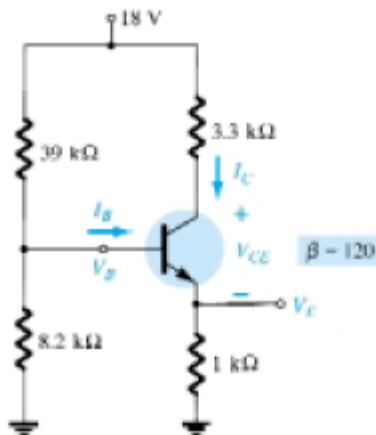


Figure 4.83 Problems 16, 17,  
21

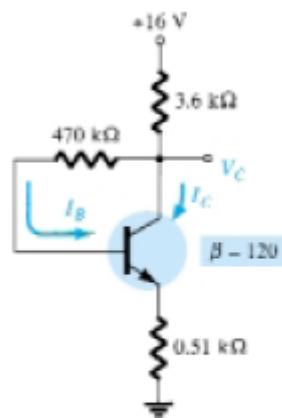- [16] (a)  $V_B=3.13\text{V}$   $I_C=2.43\text{mA}$  (b)  $V_{CE}=7.55$  (c)  $I_B=20.25\mu\text{A}$  (d)  $V_E=2.43$  (e)  $V_B=3.1$   
 [17] (a)  $I_C=2.28\text{mA}$  (b)  $V_{CE}=8.2$  (c)  $I_B=19.02\mu\text{A}$  (d)  $V_E=2.28$  (e)  $V_B=2.98$



22. For the collector feedback configuration of Fig. 4.84, determine:

- (a)  $I_B$ .
- (b)  $I_C$ .
- (c)  $V_C$ .

(a)  $I_B = 15.88\mu A$  (b)  $I_C = 1.91mA$  (c)  $V_C = V_{CC} - I_C \cdot R_C = 9.12V$

Figure 4.84 Problems 22, 50,  
56

25. Determine the range of possible values for  $V_C$  for the network of Fig. 4.87 using the 1-MΩ potentiometer.


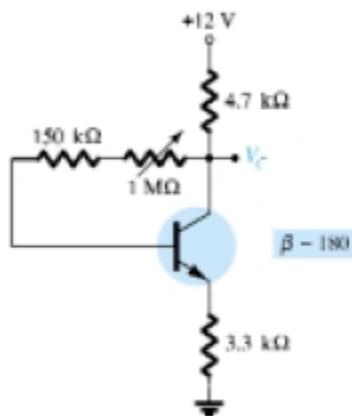


Figure 4.87 Problem 25

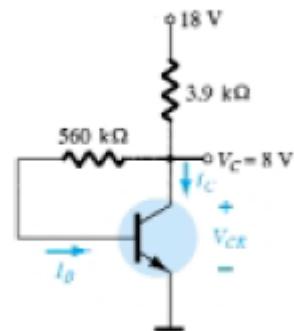(a)  $I_B = 7.11\mu A$   $I_C = 1.28mA$   $V_C = 5.98V$  (b)  $R_B = 11.5M$  pot completo  $I_B = 4.36\mu A$   $I_C = \beta \cdot I_B = 0.78mA$   
range  $V_C$  entre 5.98 e 8.31V



27. Given  $V_C = 8 V$  for the network of Fig. 4.89, determine:

- (a)  $I_B$ .
- (b)  $I_C$ .
- (c)  $\beta$ .
- (d)  $V_{CE}$ .

Figure 4.89 Problem 27

(a)  $I_B = 13.04\mu A$  (b)  $I_C = 2.56mA$  (c)  $\beta = 196.3$  (d)  $V_{CE} = 8V$

\* 28. For the network of Fig. 4.90, determine:

- (a)  $I_B$ .
- (b)  $I_C$ .
- (c)  $V_{CE}$ .
- (d)  $V_C$ .

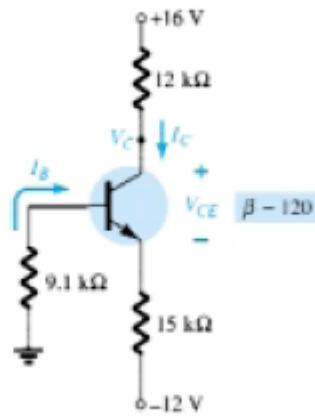


Figure 4.90 Problem 28

- (a)  $I_B=6.2\mu A$  (b)  $I_C=0.74mA$  (c)  $V_{CE}=7.91V$  (d)  $V_C=V_{CC}-I_C.R_C=7.07V$

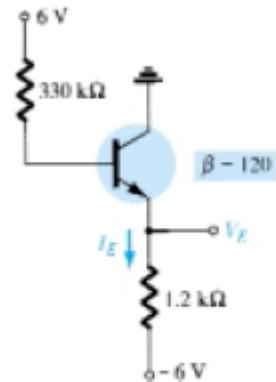


Figure 4.92 Problem 30

\* 30. Determine the level of  $V_E$  and  $I_E$  for the network of Fig. 4.92.

- (a)  $V_E=-2.54V$  e  $I_E=2.88mA$

\* 31. For the network of Fig. 4.93, determine:

- (a)  $I_E$ .
- (b)  $V_C$ .
- (c)  $V_{CE}$ .

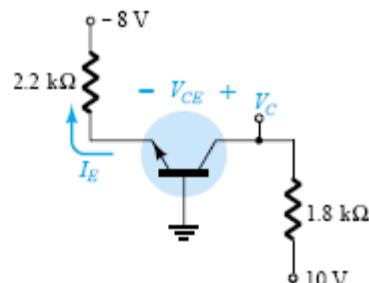


Figure 4.93 Problem 31

- (a)  $I_E=3.32mA$  (b)  $V_C=4V$  (c)  $V_{CE}=4.72$

32. Determine  $R_C$  and  $R_B$  for a fixed-bias configuration if  $V_{CC} = 12 V$ ,  $\beta = 80$ , and  $I_{CQ} = 2.5 mA$  with  $V_{CEQ} = 6 V$ . Use standard values.

$$RB=361.6K \text{ valor com } 360K \text{ e } RC=2K4$$

33. Design an emitter-stabilized network at  $I_{CQ} = \frac{1}{2}I_{Cmax}$  and  $V_{CEQ} = \frac{1}{2}V_{CC}$ . Use  $V_{CC} = 20 V$ ,  $I_{Cmax} = 10 mA$ ,  $\beta = 120$ , and  $R_C = 4R_E$ . Use standard values.

Valores comerciais RE=390 RC=1k6 RB=430K

34. Design a voltage-divider bias network using a supply of 24 V, a transistor with a beta of 110, and an operating point of  $I_{CQ} = 4 mA$  and  $V_{CEQ} = 8 V$ . Choose  $V_E = \frac{1}{4}V_{CC}$ . Use standard values.

**Observação –  $VE = VCC/8$  (figura com definição deficiente)**

Valores comerciais RE=750 RC=3K3 R1=43K R2=7K5