

**Lista III – EN2602 Prof Marcelo Perotoni, cap 7 e 8**

**OBS- Nos circuitos, desenhe sempre o modelo de pequenos sinais correspondente!!**

**Cap 7**

1. (a) What is the expected amplification of a BJT transistor amplifier if the dc supply is set to zero volts?  
 (b) What will happen to the output ac signal if the dc level is insufficient? Sketch the effect on the waveform.  
 (c) What is the conversion efficiency of an amplifier in which the effective value of the current through a 2.2-k $\Omega$  load is 5 mA and the drain on the 18-V dc supply is 3.8 mA?

3. What is the reactance of a 10- $\mu$ F capacitor at a frequency of 1 kHz? For networks in which the resistor levels are typically in the kilohm range, is it a good assumption to use the short-circuit equivalence for the conditions just described? How about at 100 kHz?

R: 15.92R para 1kHz, para 100kHz 0.1592R

**Cap 8**

1. For the network of Fig. 8.64:
  - (a) Determine  $Z_i$  and  $Z_o$ .
  - (b) Find  $A_v$  and  $A_i$ .
  - (c) Repeat part (a) with  $r_o = 20$  k $\Omega$ .
  - (d) Repeat part (b) with  $r_o = 20$  k $\Omega$ .

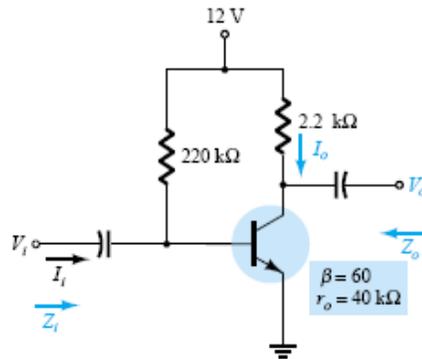


Figure 8.64 Problems 1 and 21

R: (a)  $Z_i=497.5$   $Z_o=2k2$  (b)  $A_v=-264.74$   $A_i=\beta$  (c)  $Z_i$  o mesmo antes,  $Z_o=1.98K$  (d)  $A_v=-238.27$  e  $A_i=53.88$

2. For the network of Fig. 8.65, determine  $V_{CC}$  for a voltage gain of  $A_v = -200$ .

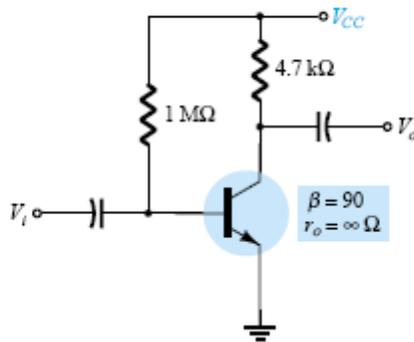


Figure 8.65 Problem 2

R:  $V_{cc}=12.85$

4. For the network of Fig. 8.67:
- Determine  $r_e$ .
  - Calculate  $Z_i$  and  $Z_o$ .
  - Find  $A_v$  and  $A_f$ .
  - Repeat parts (b) and (c) with  $r_o = 25 \text{ k}\Omega$ .

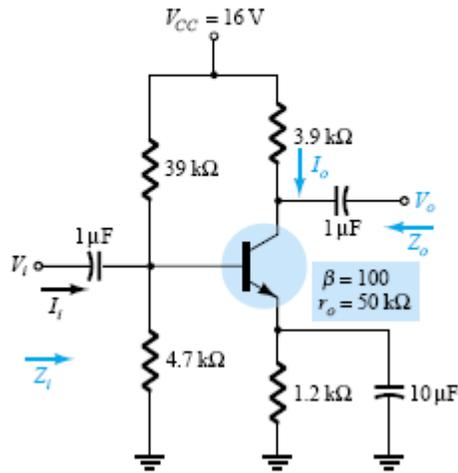


Figure 8.67 Problem 4

R: (a)  $r_e=30.56$  (b)  $Z_i=1.768\text{k}$  e  $Z_o=3\text{k}9$  (c)  $A_v=-127.6$   $A_i=57.85$  (d)  $A_v=-110.28$   $A_i=50$

5. Determine  $V_{CC}$  for the network of Fig. 8.68 if  $A_v = -160$  and  $r_o = 100 \text{ k}\Omega$ .


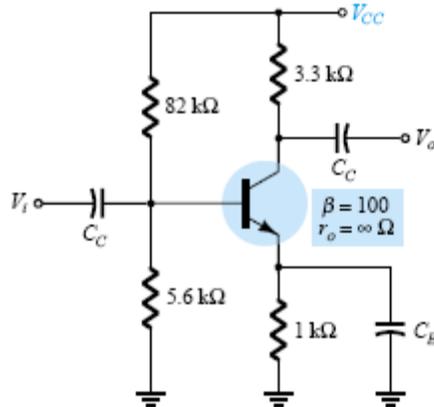


Figure 8.68 Problem 5

R:  $V_{cc}=30.68$

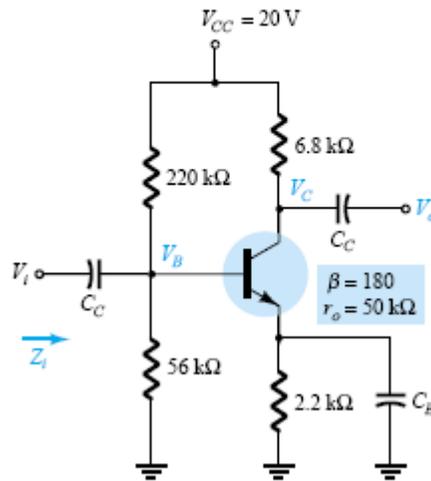6. For the network of Fig. 8.69:
- Determine  $r_e$ .
  - Calculate  $V_B$  and  $V_C$ .
  - Determine  $Z_i$  and  $A_v = V_o/V_i$ .



R: (a)  $r_e=18.95$  (b)  $V_b=3.72$  e  $V_c=10.72$  (c)  $Z_i=3.17k$  e  $A_v=-315.88$

7. For the network of Fig. 8.70:
- Determine  $r_e$ .
  - Find  $Z_i$  and  $Z_o$ .
  - Calculate  $A_v$  and  $A_i$ .
  - Repeat parts (b) and (c) with  $r_o = 20 \text{ k}\Omega$ .

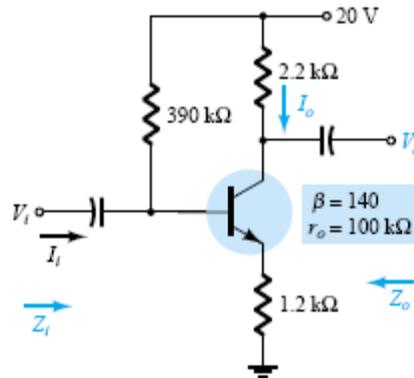


Figure 8.70 Problems 7 and 9

R: (a)  $r_e=5.34$  (b)  $Z_o=2200$  e  $Z_i=118.37$  (c)  $A_v=-1.82$  (d)  $A_v=-1.81$   $A_i=87.17$

- \* 10. For the network of Fig. 8.72:
- Determine  $r_e$ .
  - Find  $Z_i$  and  $A_v$ .
  - Calculate  $A_i$ .


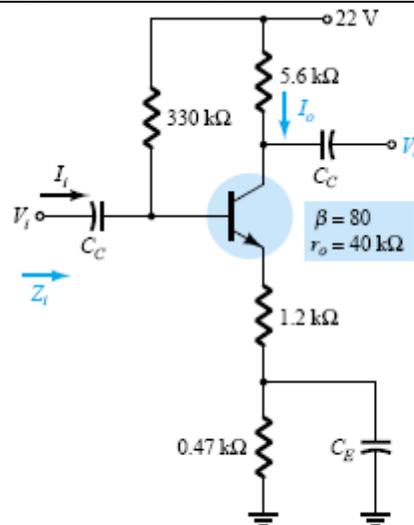


Figure 8.72 Problem 10

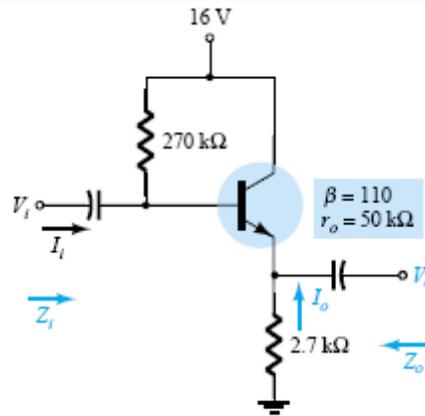R: (a)  $r_e=7$  (b)  $Z_i=66.82k$   $A_v=-4.57$  (c)  $A_i=54.53$



11. For the network of Fig. 8.73:

- Determine  $r_e$  and  $\beta r_e$ .
- Find  $Z_i$  and  $Z_o$ .
- Calculate  $A_v$  and  $A_i$ .

Figure 8.73 Problem 11

(a)  $r_e=8.72$  (b)  $Z_i=142.25k$   $Z_o=8.69$  (c)  $A_v=0.997$   $A_i=-52.3$

14. For the common-base configuration of Fig. 8.76:

- Determine  $r_e$ .
- Find  $Z_i$  and  $Z_o$ .
- Calculate  $A_v$  and  $A_i$ .

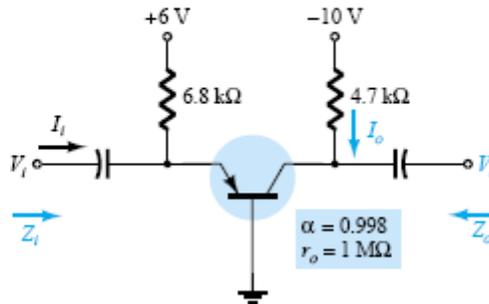


Figure 8.76 Problem 14

(a)  $r_e=33.38$  (b)  $Z_i=33.22$   $Z_o=4K7$  (c)  $A_v=\alpha \cdot R_e/r_e=140.52$   $A_i=-\alpha=-0.998$

\* 15. For the network of Fig. 8.77, determine  $A_v$  and  $A_i$ .

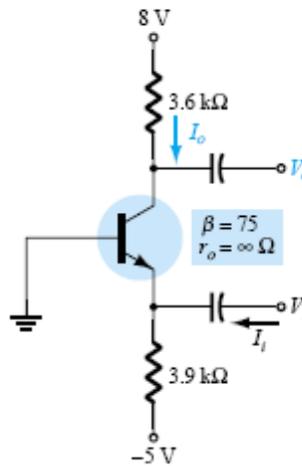


Figure 8.77 Problem 15

R: (a)  $A_v=163.2$   $A_i=-\alpha=-0.968$

16. For the collector FB configuration of Fig. 8.78:

- (a) Determine  $r_e$ .
- (b) Find  $Z_i$  and  $Z_o$ .
- (c) Calculate  $A_v$  and  $A_i$ .


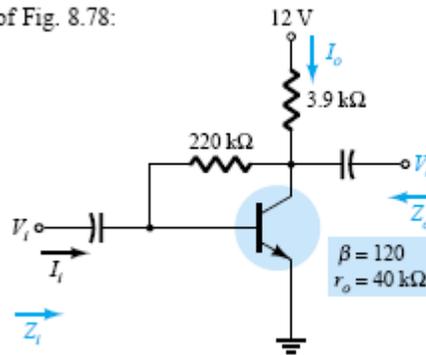


Figure 8.78 Problem 16

R: (a)  $r_e=10.08$  (b) usa formula aproximada para  $Z_i=498$   $Z_o=3k83$  (c)  $A_v=-298$   $A_i=38.37$

### Sedra Smith, 5ª edição

**D5.56** Consider the CE amplifier circuit of Fig. 5.26(a) when operated with a dc supply  $V_{CC} = +5$  V. It is required to find the point at which the transistor should be biased; that is, find the value of  $V_{CE}$  so that the output sine-wave signal  $v_o$  resulting from an input sine-wave signal  $v_{be}$  of 5-mV peak amplitude has the maximum possible magnitude. What is the peak amplitude of the output sine wave and the value of the gain obtained? Assume linear operation around the bias point. (*Hint*: To obtain the maximum possible output amplitude for a given input, you need to bias the transistor as close to the edge of saturation as possible without entering saturation at any time, that is, without  $v_{CE}$  decreasing below 0.3 V.)

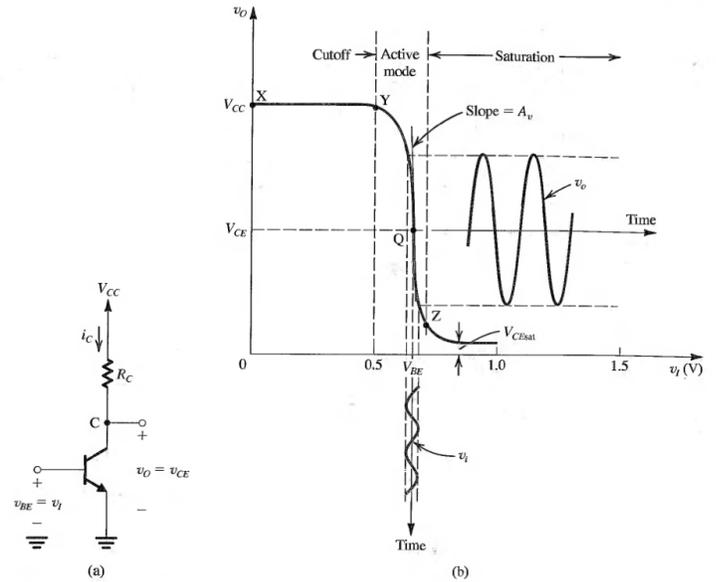

**FIGURE 5.26** (a) Basic common-emitter amplifier circuit. (b) Transfer characteristic of the circuit in (a). The amplifier is biased at a point Q, and a small voltage signal  $v_i$  is superimposed on the dc bias voltage  $V_{BE}$ . The resulting output signal  $v_o$  appears superimposed on the dc collector voltage  $V_{CE}$ . The amplitude of  $v_o$  is larger than that of  $v_i$  by the voltage gain  $A_v$ .

R:  $A_v=-156.67$  **Nota:**  $V_T$  para esse autor é 25mV

Dica: Esboce a saída grafica da tensão total no coletor, deve ser uma soma da tensão DC quiescente + ganho, no ponto mais baixo o sinal deve ser maior ou igual a 0.3V. Depois expresse o ganho do emissor comum da figura em função de  $R_c, I_c$  e  $V_t$  e o resultado irá aparecer, considerando a tensão mínima como sendo obrigatoriamente 0.3V.

**5.57** The transistor in the circuit of Fig. P5.57 is biased at a dc collector current of 0.5 mA. What is the voltage gain? (*Hint*: Use Thévenin theorem to convert the circuit to the form in Fig. 5.26a).

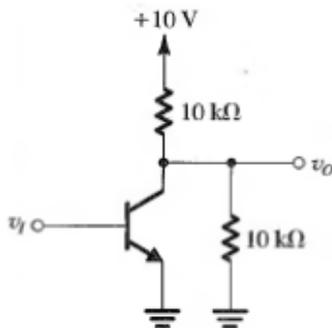


FIGURE P5.57

Dica: por Thevenin, entenda simplesmente o paralelo de  $R_c$  com  $R_l$ . Use as considerações do exercício acima e a resposta sai fácil.

R:  $A_v=-100$