

Lista IV EN2719 Prof Marcelo Perotoni

1. For the fixed-bias configuration of Fig. 6.67:
 - (a) Sketch the transfer characteristics of the device.
 - (b) Superimpose the network equation on the same graph.
 - (c) Determine I_{DQ} and V_{DSQ} .
 - (d) Using Shockley's equation, solve for I_{DQ} and then find V_{DSQ} . Compare with the solutions of part (c).

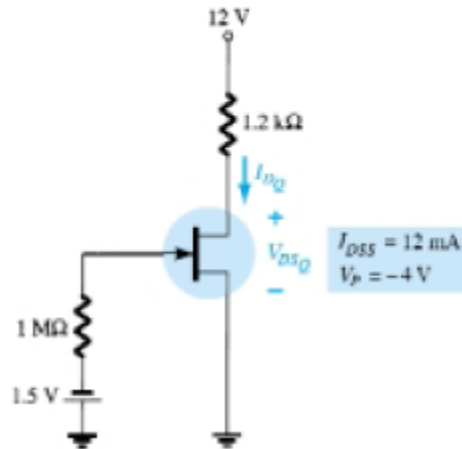


Figure 6.67 Problems 1, 35

Observação – ignore o pedido de solução gráfica, resolva o ponto quiescente apenas pela equação de Schockley
R: $V_{gs}=1.5V$ e $I_{dq}=4.68mA$, $V_{dsq}=6.48$

3. Given the measured value of V_D in Fig. 6.69, determine:
 - (a) I_D .
 - (b) V_{DS} .
 - (c) V_{GG} .

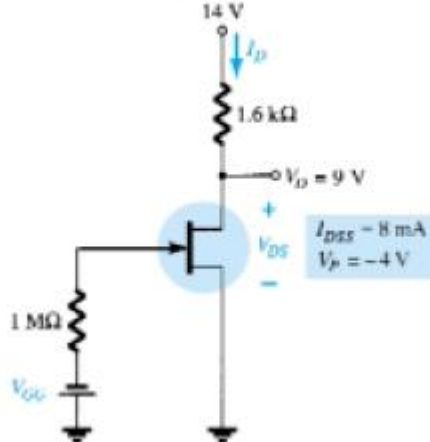


Figure 6.69 Problem 3

R: (a) $I_{dq}=3.125mA$ (b) $V_{ds}=9$ (c) $V_{gg}=1.5V$

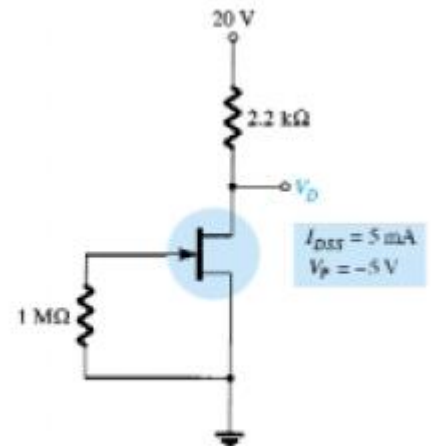


Figure 6.70 Problem 4

4. Determine V_D for the fixed-bias configuration of Fig. 6.70.

R: (a) $I_{dq}=5mA$ $V_d=9$

- * 7. Determine I_{DQ} for the network of Fig. 6.72 using a purely mathematical approach. That is, establish a quadratic equation for I_D and choose the solution compatible with the network characteristics. Compare to the solution obtained in Problem 6.

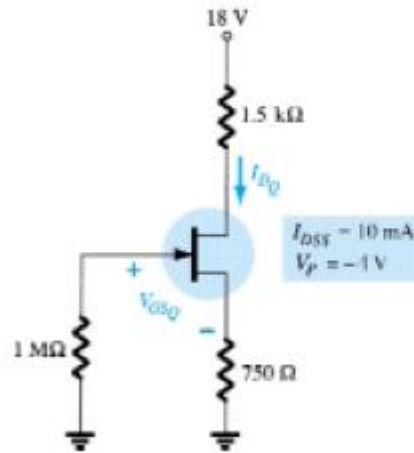


Figure 6.72 Problems 6, 7, 36

Observação – ignore o pedido de comparação com solução gráfica (problema 6)

R: (a) $I_{DQ}=2.6\text{mA}$ $V_{GS}=-1.95$

8. For the network of Fig. 6.73, determine:

- (a) V_{GSQ} and I_{DQ}
 (b) V_{DS} , V_D , V_G , and V_S .

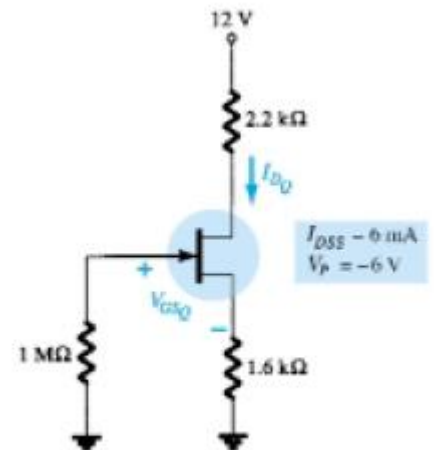


Figure 6.73 Problem 8

R: (a) $I_{DQ}=1.73\text{mA}$ (b) $V_{GS}=-2.76$ $V_{DS}=5.42$ $V_D=8.19$ $V_S=2.77$ $V_G=0$

- * 10. For the network of Fig. 6.75, determine:

- (a) I_D
 (b) V_{DS}
 (c) V_D
 (d) V_S .

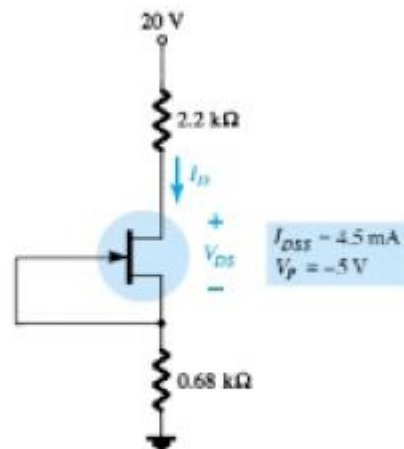


Figure 6.75 Problem 10

R: (a) $I_{DQ}=I_{DSS}=4.5\text{mA}$ (b) $V_{DS}=7.04$ (c) $V_D=10.1\text{V}$ (d) $V_S=3.06$

- * 11. Find V_S for the network of Fig. 6.76.

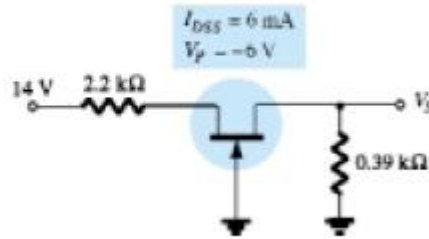


Figure 6.76 Problem 11

R: (a) $I_{DQ}=3.55\text{mA}$ $V_S=1.38\text{V}$

12. For the network of Fig. 6.77, determine:

- (a) V_G .
 (b) I_{DQ} and V_{GSQ} .
 (c) V_D and V_S .
 (d) V_{DSQ} .

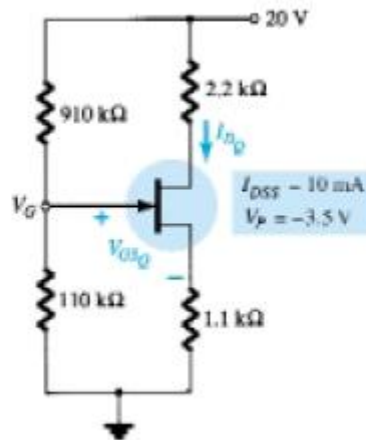


Figure 6.77 Problems 12, 13

Façam esse, matematicamente! Vão ter que ralar miúdo e pensar um pouco. Quer coisa me consultem

R: $I_{DQ}=3.3\text{mA}$ $V_G=2.13$ $I_{DQ}=3.3\text{mA}$ $V_{GSQ}= -1.5$ $V_D=12.74\text{V}$ $V_S=3.63$ $V_{DSQ}=9.11$

- * 16. Given $V_{DS} = 4 \text{ V}$ for the network of Fig. 6.80, determine:

- (a) I_D .
 (b) V_D and V_S .
 (c) V_{GS} .

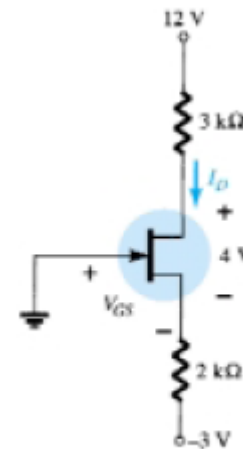


Figure 6.80 Problem 16

R: (a) $I_{DQ}=2.2\text{mA}$ (b) $V_D=5.4\text{V}$ $V_S=1.4\text{V}$ (c) $V_{GS}=-1.4\text{V}$

- * 23. Design a self-bias network using a JFET transistor with $I_{DSS} = 8 \text{ mA}$ and $V_P = -6 \text{ V}$ to have a Q -point at $I_{DQ} = 4 \text{ mA}$ using a supply of 14 V . Assume that $R_D = 3R_S$ and use standard values.

R: $V_{GS}=-1.75\text{V}$ $R_S=440 \text{ Ohms}$ e $R_D=1\text{K}32$