

Lista V EN2602 Prof Marcelo Perotoni, cap 9

OBS – Mostre o modelo de pequenos sinais para cada caso. Procure, sempre que possível, deduzir as fórmulas de impedância e ganho usadas!!

17. Determine Z_i , Z_o and A_v for the network of Fig. 9.54 if $I_{DSS} = 10 \text{ mA}$, $V_p = -4 \text{ V}$, and $r_d = 40 \text{ k}\Omega$.

18. Determine Z_i , Z_o , and A_v for the network of Fig. 9.54 if $I_{DSS} = 12 \text{ mA}$, $V_p = -6 \text{ V}$, and $y_{os} = 40 \mu\text{S}$.

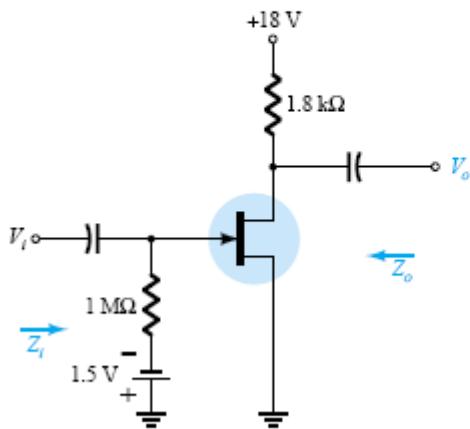


Figure 9.54 Fixed-bias amplifier for Problems 17 and 18

$$\text{R: 17. } Z_i=1\text{M}, Z_o=1.72\text{K } A_v=-5.375$$

$$\text{R: 18. } Z_i=1\text{M}, Z_o=1.68\text{K } A_v=-5.04$$

20. Determine Z_i , Z_o and A_v for the network of Fig. 9.56 if $I_{DSS} = 6 \text{ mA}$, $V_p = -6 \text{ V}$, and $y_{os} = 40 \mu\text{S}$.

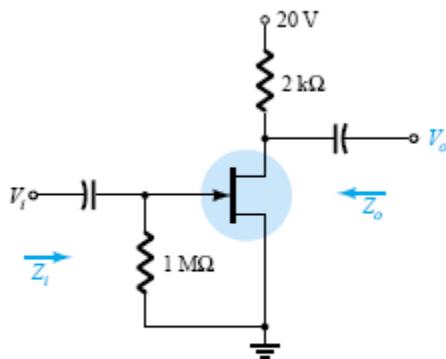


Figure 9.56 Self-bias configuration for Problems 20 and 47

$$\text{R: } Z_i=1\text{M}, Z_o=1852 \text{ Ohms } A_v=-3.7$$

23. Determine Z_i , Z_o , and V_o for the network of Fig. 9.57 if $V_i = 20 \text{ mV}$.


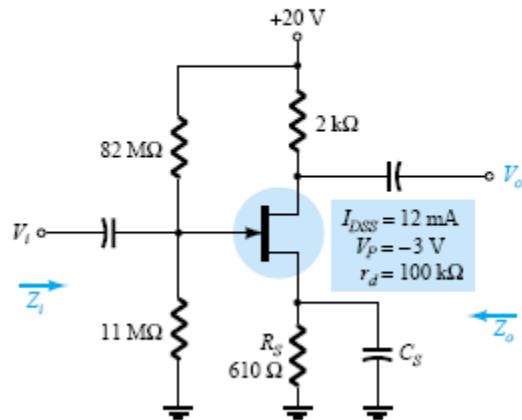


Figure 9.57 Problems 23–26 and 48

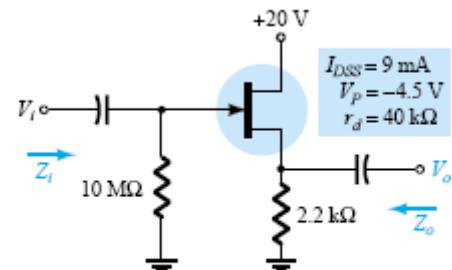R: $I_d = 5.46 \text{ mA}$ $Z_i = 9.7 \text{ M}\Omega$, $Z_o = 2 \text{ k}\Omega$ $A_v = -10.94$



27. Determine Z_i , Z_o , and A_v for the network of Fig. 9.58.

28. Repeat Problem 27 if $r_d = 20 \text{ k}\Omega$.

R: 27. $I_d = 1.25 \text{ mA}$ $Z_i = 10 \text{ M}\Omega$, $Z_o = 512.9 \text{ k}\Omega$ $A_v = 0.754$

R: 28. $I_d = 1.25 \text{ mA}$ $Z_i = 10 \text{ M}\Omega$, $Z_o = 506.4 \text{ k}\Omega$ $A_v = 0.745$

30. Determine Z_i , Z_o , and V_o for the network of Fig. 9.60 if $V_i = 0.1 \text{ mV}$.

31. Repeat Problem 30 if $r_d = 25 \text{ k}\Omega$.


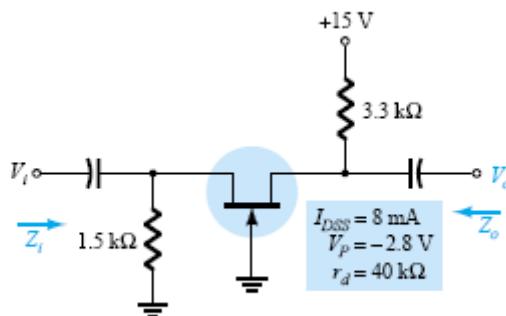


Figure 9.60 Problems 30, 31, and 49

R: 30. $I_d = 1.1568 \text{ mA}$ $Z_i = 356.3 \text{ k}\Omega$, $Z_o = 3 \text{ k}\Omega$ $A_v = 7.06$

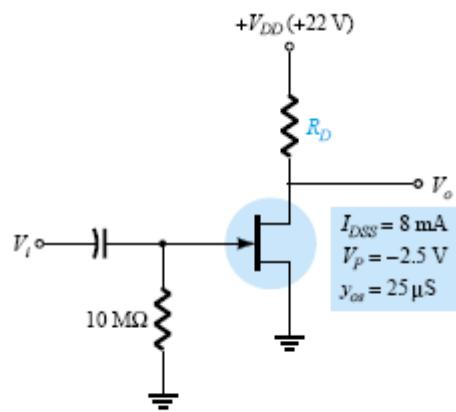R: 31 (aqui devo usar formulas AC exatas, rd bem menor). $Z_i = 386.12 \text{ k}\Omega$, $Z_o = 2.92 \text{ k}\Omega$ $A_v = 6.36$



44. Design the fixed-bias network of Fig. 9.69 to have a gain of 8.

Figure 9.69 Problem 44

R: Rd=1290 Ohms com rd=40K e gm=gm0=64mS

45. Design the self-bias network of Fig. 9.70 to have a gain of 10. The device should be biased at $V_{GSQ} = \frac{1}{3}V_P$.

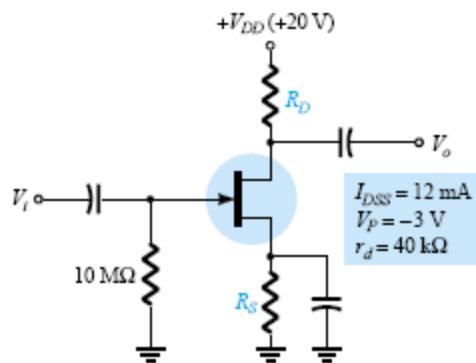


Figure 9.70 Problem 45

R: Id=5.33mA Rd=1970 Ohms e Rs=187.62 Ohms