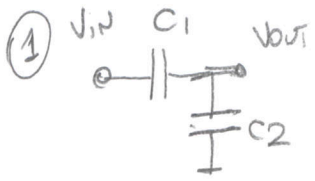


APLICADA P1 2017.2



(a)  $\left| \frac{V_{out}}{V_{in}} \right| = \frac{|X_{C2}|}{|X_{C1} + X_{C2}|} = \frac{1/j\omega C2}{\frac{1}{j\omega C2} + \frac{1}{j\omega C1}} = \frac{1/j\omega C2}{\frac{j\omega C1 + j\omega C2}{(j\omega C2)(j\omega C1)}}$

$\frac{V_{out}}{V_{in}} = \frac{1}{j\omega C2} \cdot \frac{j\omega C2 \cdot j\omega C1}{j\omega C1 + j\omega C2} = \frac{C1}{C1 + C2} = \frac{10}{127}$

escolha p/ ex  $C2 = 10 \mu F \rightarrow 127 C1 = 10(C1 + 10) \rightarrow C1 = \frac{100}{117} \mu F$



(b) Relação  $\frac{V_{out}}{V_{in}} = \frac{C1}{C1 + C2}$  logo independente da frequência; relação seria a mesma!

(2) (a)  $C_M = (A_V + 1) A_V$  se INVERTOR  $A_V \approx \frac{R_C}{R_E} = \frac{99K}{100} = 99$

$C_M = (99 + 1) \cdot 1pF = 100pF$


(b) polo altas f:  $\frac{1}{2\pi R C_M} = \frac{1}{2\pi \cdot (100 \cdot 100) \cdot 100E-12} = 159 KHZ$

$Z_{in} = \beta R_E = 100 \cdot 100$

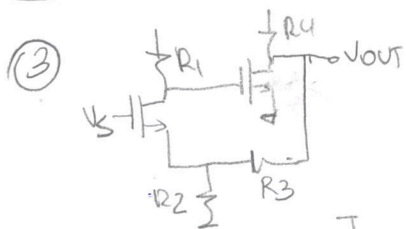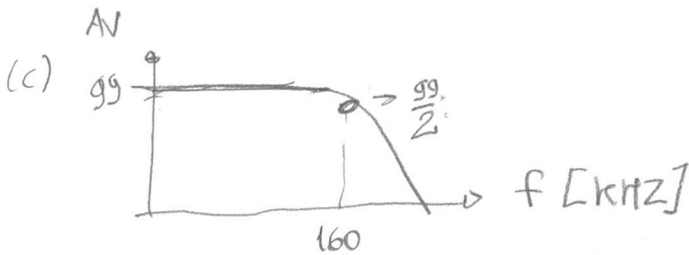

(a) Análise V Compens V  
Análise V  $\rightarrow$  CKT INAPT MAKE  $V_b = 0$   
Compens V  $\rightarrow$  CKT APART MAKE  $I_i = 0$


(c) Formula  
 $A_{V \text{ STAGE \#1}} = \frac{-g_m R_D}{1 + g_m R_S} = \frac{-g_m R_1}{1 + g_m (R_2 || R_3)} = -8.7$

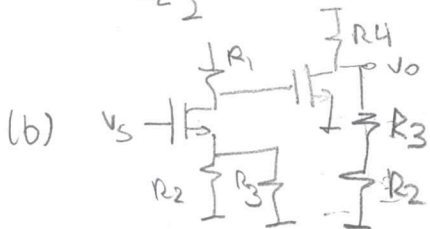

$A_{V \text{ STAGE \#2}} = -g_m R_4 / [R_2 + R_3] = -20$

$$A_{V_{TOTAL}} = A_{V_{STAGE\#1}} \cdot A_{V_{STAGE\#2}} = -8.7 \cdot -20 = 174 \text{ V/V}$$

(d)  $\beta = \frac{V_F}{V_O}$

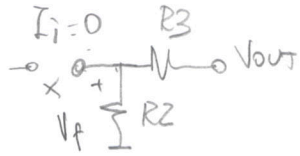


$$V_F = V_{out} \cdot \frac{R_2}{R_3 + R_2} = \frac{9000}{10000} = 0.9$$

$$\beta = \frac{V_F}{V_{out}} = 0.9$$

$$A_{VF} = \frac{A}{1 + \beta A} = \frac{174}{1 + 174(0.9)} = 1.10 \text{ V/V}$$

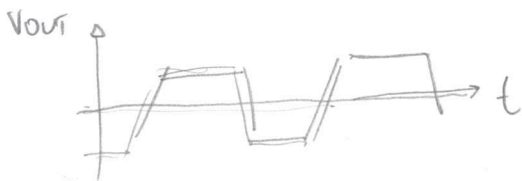(4) (a) OBT possui capacitores nos drenários passar o nível DC da onda.



(b)  $t_r = t_f = 1 \text{ ns}$   
transistor


$BW \approx \frac{0.35}{1 \text{ ns}} = 350 \text{ MHz}$   
não responde



↑ problema nos altos

(c) Achar K com  $f_T$  maior  
aumentar  $I_{CQ}$  e  $R_{MAX}$

(5)

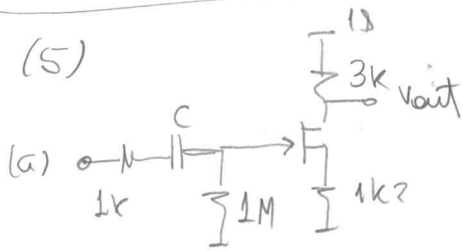


$$\frac{V_{out}}{V_{in}} = -g_m \frac{R_o}{1 + g_m R_s}$$

$$V_p = -6 \quad V_{avg} = -2.45 \text{ V}$$

$$g_m = g_{m0} \left[ 1 - \frac{V_{CEQ}}{V_p} \right] = \frac{2 I_{CQ}}{V_p} \left[ 1 - \frac{(-2.45)}{(-6)} \right] = 1.18 \text{ mS}$$


$$A_{medias} = -1.18 \frac{3}{1 + 1.18 \cdot 1.2} = 1.46$$

(b) polo  $C = 1 \mu\text{F}$

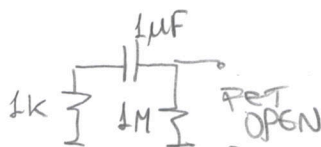

$$f_L = \frac{1}{2\pi(1\text{M} + 1\text{k})1\mu\text{F}} \approx 0.159 \text{ Hz}$$

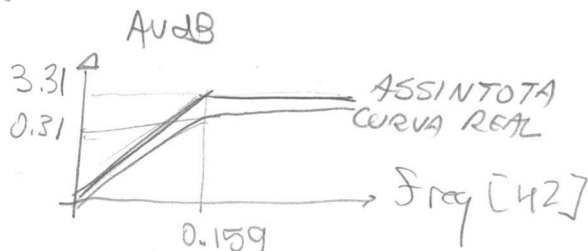(c)  $A_{VL_{dB}} = 20 \log 1.46 = 3.31 \text{ dB}$



PI-2  
2017.2