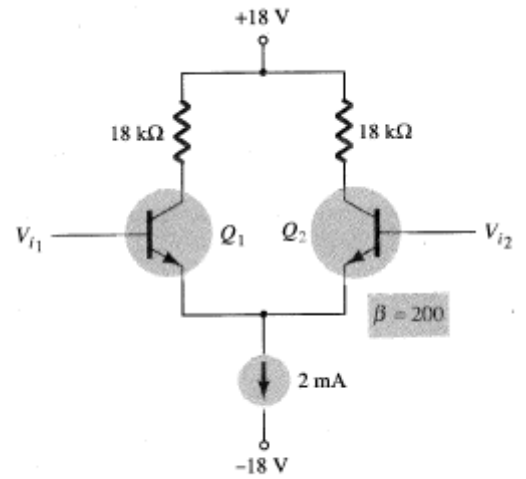


26. Calcule os valores de I_C e V_C para os transistores casados da Fig. 12.76.

Fig. 12.76 Problema 26.


R: ($I_C=1.5\text{mA}$, $V_C=7.95\text{V}$)



27. Calcule os valores de I_C e V_C para os transistores casados da Fig. 12.77.

Fig. 12.77 Problema 27.


R: ($I_C=1\text{mA}$, $V_C=0\text{V}$)

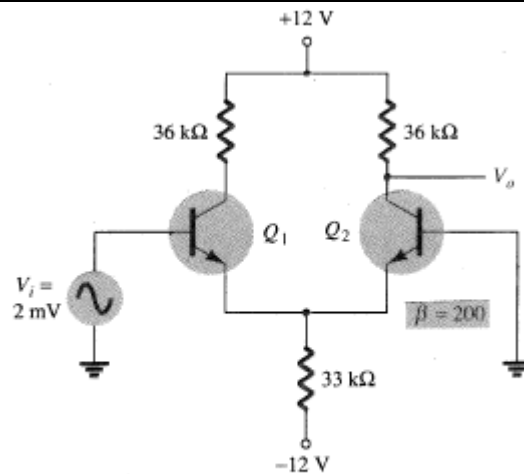

*28. Calcule V_o no circuito da Fig. 12.78.

Fig. 12.78 Problema 28.

R: $V_o=236.8\text{mV}$

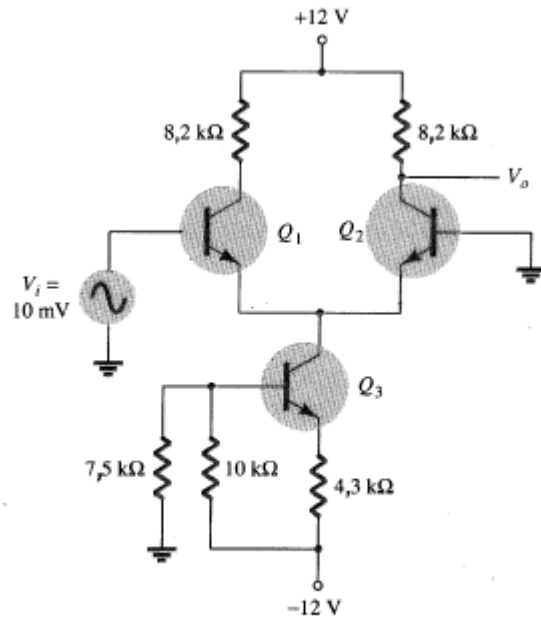

*29. Calcule V_o no circuito da Fig. 12.79.

Fig. 12.79 Problema 29.

R: 2.25V

**Dica: Q3 se comporta como fonte de corrente. Calcule, via divisor de tensão (7K5 e 10K) a tensão na base de Q3. Em seguida, aplique KVL na malha Base – Junção BE – fonte negativa Vee, achando a tensão no emissor de Q3. Sabendo essa tensão, calcule a corrente no resistor de 4K3, determinando assim a corrente fixa que é puxada do par diferencial.*

cap 14

1. Calculate the CMRR (in dB) for the circuit measurements of $V_d = 1 \text{ mV}$, $V_o = 120 \text{ mV}$, and $V_c = 1 \text{ mV}$, $V_e = 20 \text{ } \mu\text{V}$.

R: CMRR=75.56dB

2. Determine the output voltage of an op-amp for input voltages of $V_{i1} = 200 \text{ } \mu\text{V}$ and $V_{i2} = 140 \text{ } \mu\text{V}$. The amplifier has a differential gain of $A_d = 6000$ and the value of CMRR is:
 - (a) 200.
 - (b) 10^5 .

R: (a) 365mV (b) 360mV

3. What is the output voltage in the circuit of Fig. 14.44?


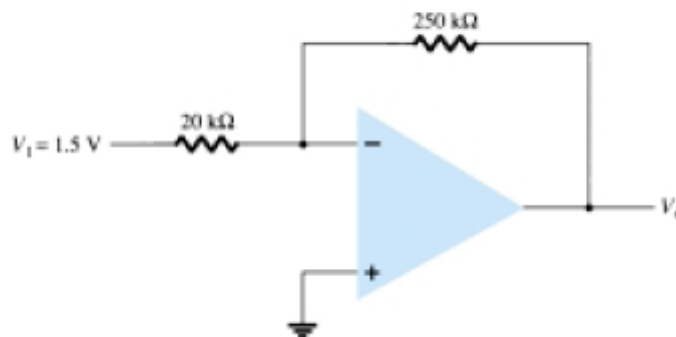


Figure 14.44 Problems 3 and 25

R: -18.75V

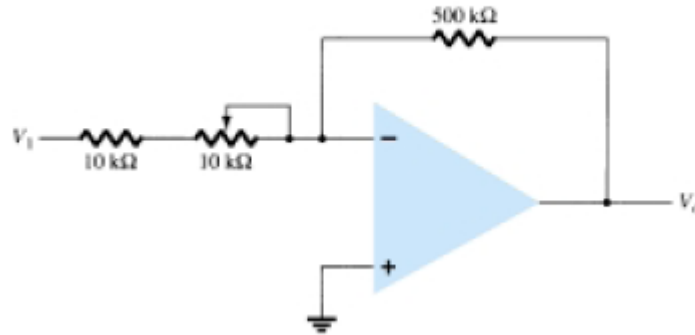4. What is the range of the voltage-gain adjustment in the circuit of Fig. 14.45?



R: ganho entre -25 e -50

5. What input voltage results in an output of 2 V in the circuit of Fig. 14.46?

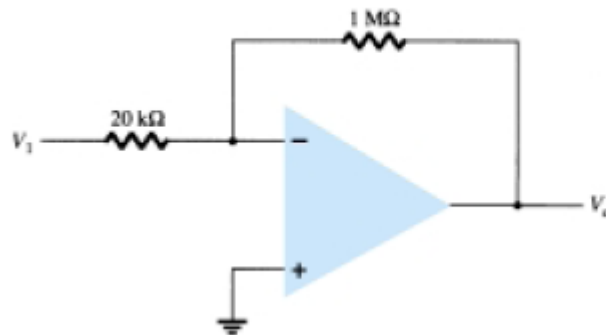


Figure 14.46 Problem 5

R: -40mV

6. What is the range of the output voltage in the circuit of Fig. 14.47 if the input can vary from 0.1 to 0.5 V?

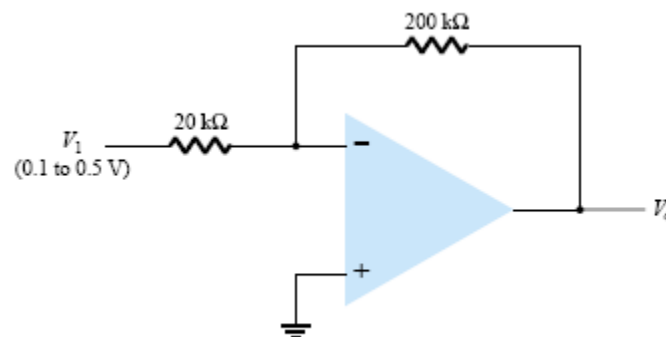


Figure 14.47 Problem 6

R: Vo esta entre [-5, -1] V

7. What output voltage results in the circuit of Fig. 14.48 for an input of $V_1 = -0.3$ V?

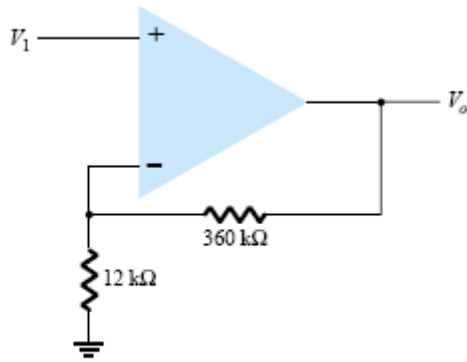


Figure 14.48 Problems 7, 8, and 26

R: $V_o = -9.3V$

8. What input must be applied to the input of Fig. 14.48 to result in an output of 2.4 V?

R: $V_i = 77.42mV$

9. What range of output voltage is developed in the circuit of Fig. 14.49?

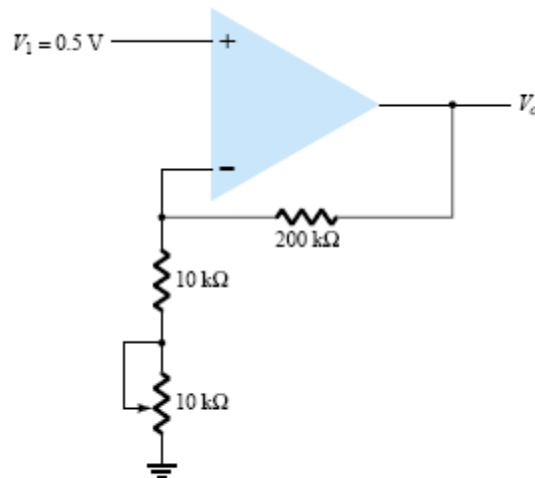


Figure 14.49 Problem 9

R: V_o entre $[5.5, 11.5] V$

10. Calculate the output voltage developed by the circuit of Fig. 14.50 for $R_f = 330 k\Omega$.

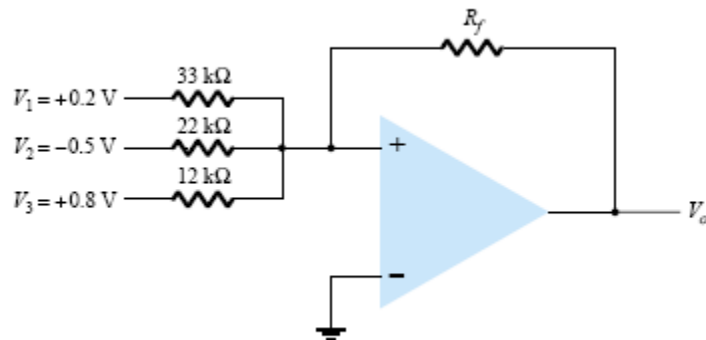


Figure 14.50 Problems 10, 11, and 27

R: $V_o = -16.5V$

Nota: Os terminais estão invertidos no desenho! A entrada inversora e não inversora devem ser intercambiadas (+ vira menos e vice versa)!!

11. Calculate the output voltage of the circuit in Fig. 14.50 for $R_f = 68 k\Omega$.

R: $V_o = -3.39V$

12. Sketch the output waveform resulting in Fig. 14.51.

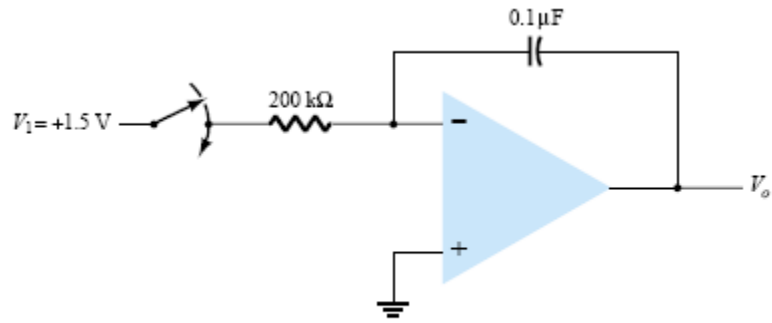


Figure 14.51 Problem 12

R: $V_o = -75t$ (considere em $t=0$ a chave fechada, logo input=1.5V constante).

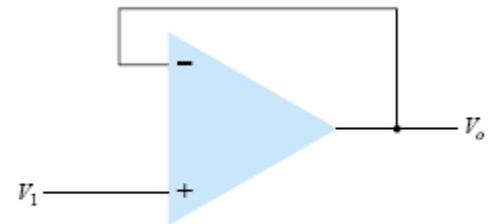


Figure 14.52 Problem 13

13. What output voltage results in the circuit of Fig. 14.52 for $V_1 = +0.5$ V?

R: $V_o = 0.5$ (configuração buffer)

14. Calculate the output voltage for the circuit of Fig. 14.53.

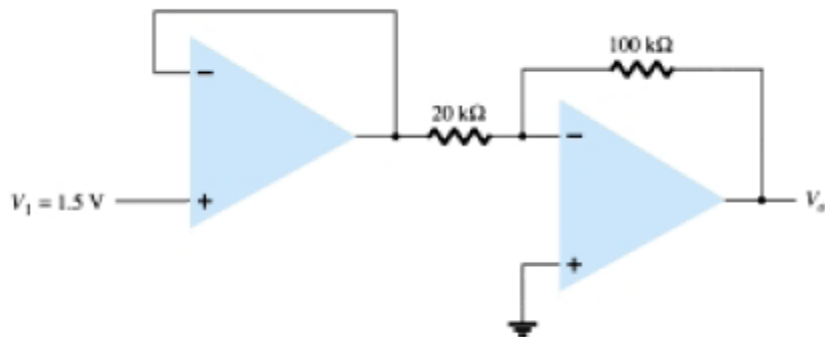


Figure 14.53 Problems 14 and 28

R: $V_o = -7.5V$

15. Calculate the output voltages V_2 and V_3 in the circuit of Fig. 14.54.

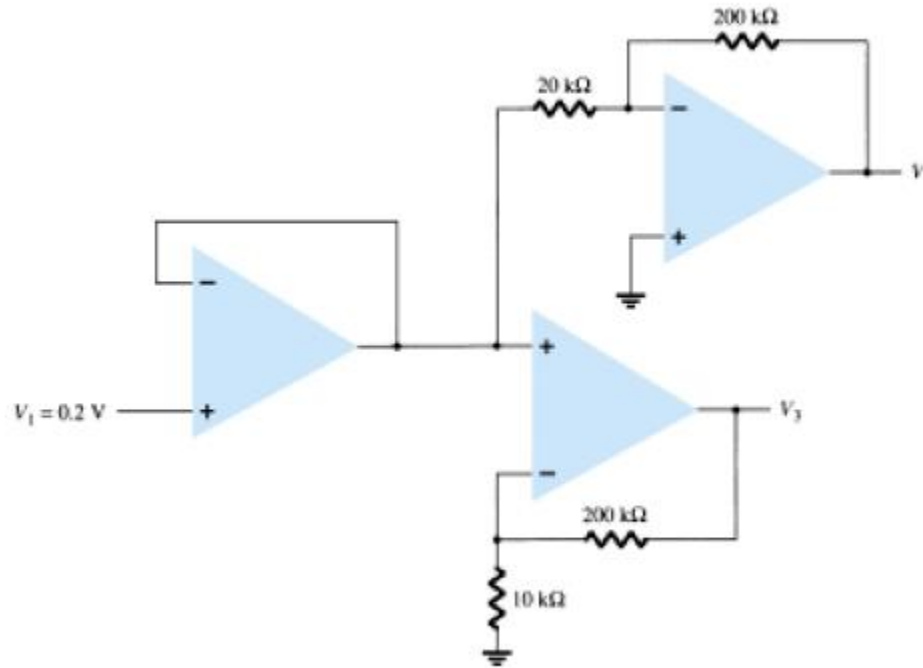


Figure 14.54 Problem 15

R: $V_2 = -2V$ e $V_3=4.2V$

16. Calculate the output voltage, V_o , in the circuit of Fig. 14.55.

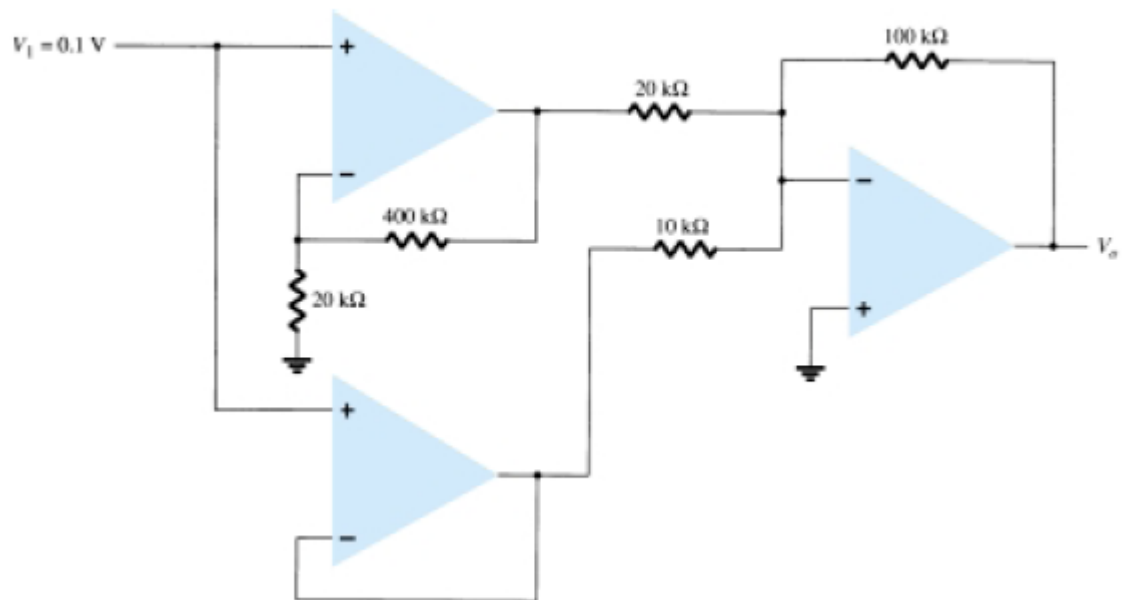


Figure 14.55 Problems 16 and 29

R: $V_o = -11.5V$

17. Calculate V_o in the circuit of Fig. 14.56.

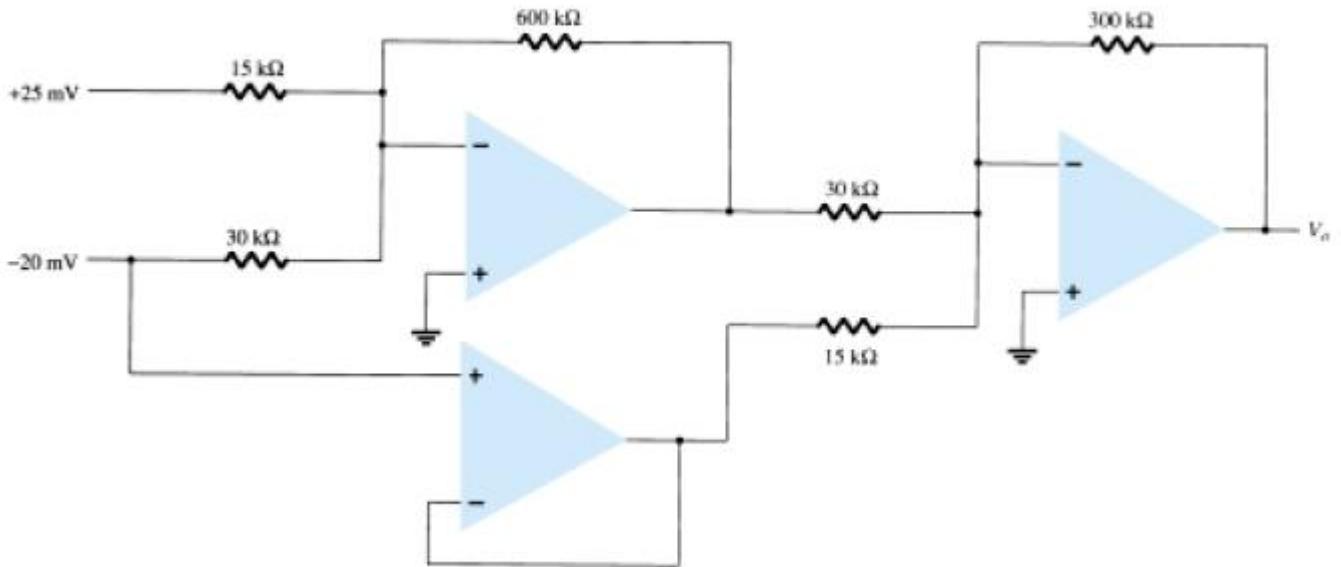


Figure 14.56 Problem 17

R: $V_o = 6.4V$

20. Determine the cutoff frequency of an op-amp having specified values $B_1 = 800 \text{ kHz}$ and $A_{VD} = 150 \text{ V/mV}$.

R: $f_c = 5.3\text{Hz}$

21. For an op-amp having a slew rate of $SR = 2.4 \text{ V}/\mu\text{s}$, what is the maximum closed-loop voltage gain that can be used when the input signal varies by 0.3 V in $10 \mu\text{s}$?

R: $A_v \text{ closed loop maximo} = 80$

22. For an input of $V_1 = 50 \text{ mV}$ in the circuit of Fig. 14.57, determine the maximum frequency that may be used. The op-amp slew rate $SR = 0.4 \text{ V}/\mu\text{s}$.

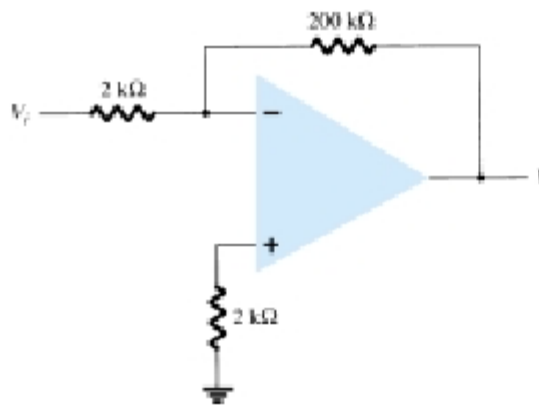


Figure 14.57 Problems 18, 22, 23, and 24

R: 12.73kHz

Nota: verifique a equação 14.24 para resolver este exercicio

cap 15

7. Determine the output voltage for the circuit of Fig. 15.52.

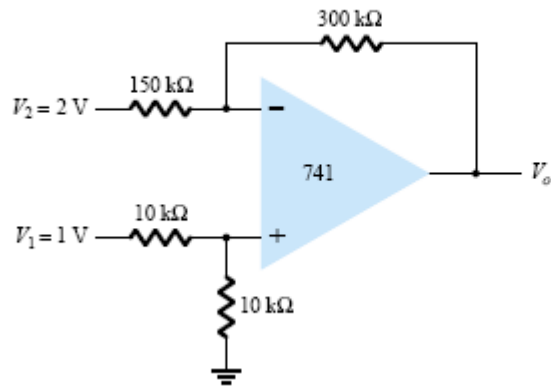


Figure 15.52 Problem 7

R: -2.5V

8. Determine the output voltage for the circuit of Fig. 15.53.


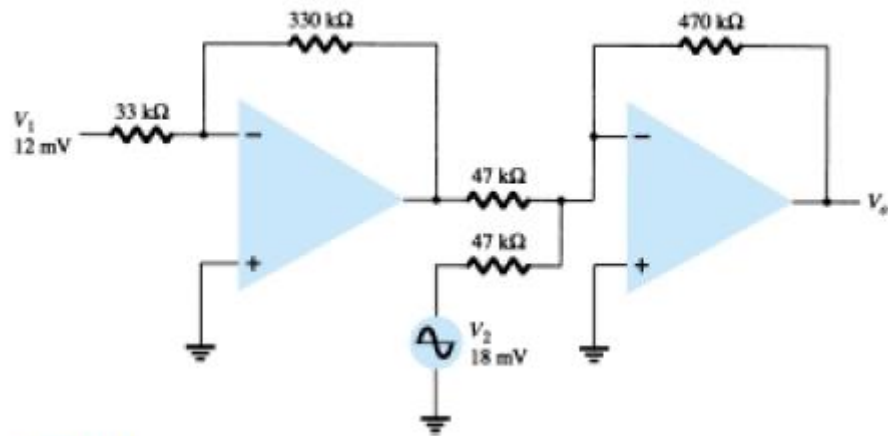



Figure 15.53 Problem 8

R: 1.02V

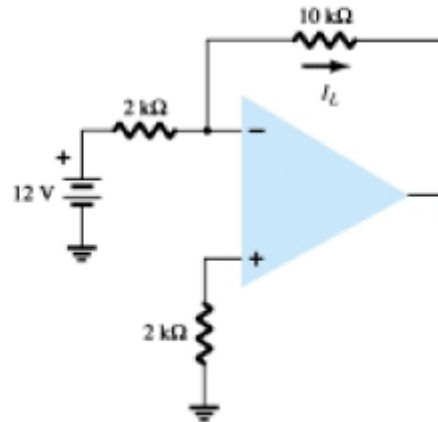

11. For the circuit of Fig. 15.54, calculate I_L . Figure 15.54 Problem 11

R: 6mA

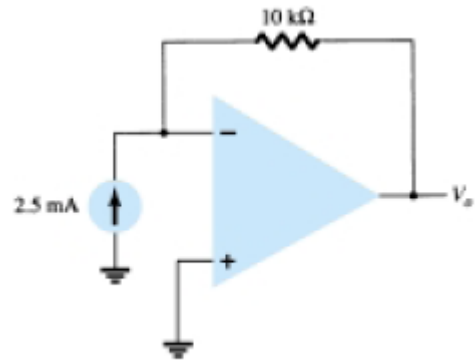

12. Calculate V_o for the circuit of Fig. 15.55. Figure 15.55 Problem 12

R: -25V

13. Calculate the output current I_o in the circuit of Fig. 15.56.

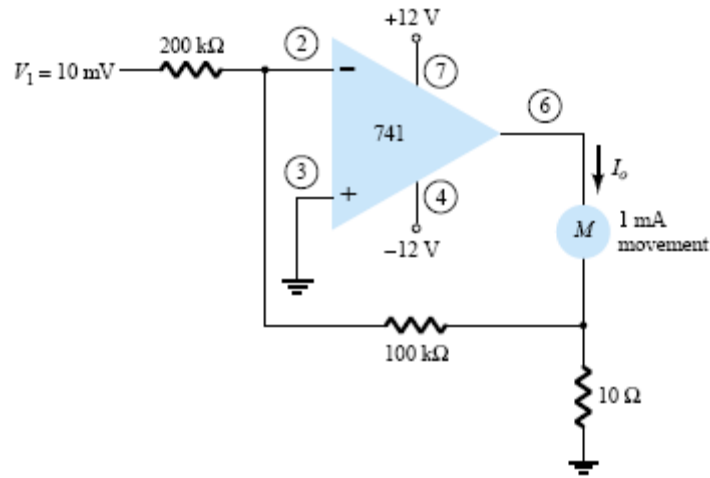


Figure 15.56 Problem 13

R: 0.5mA

*14. Calculate V_o in the circuit of Fig. 15.57.

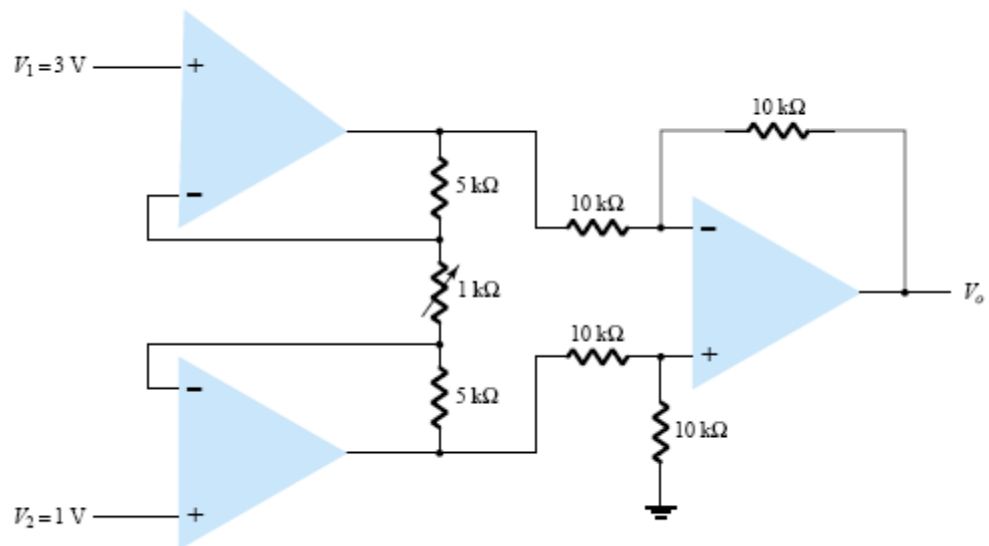



Figure 15.57 Problem 14

R: -22V

Nota: Não pode usar a fórmula pronta apresentada no livro; o circuito é diferente. Ache a equação calculando as

tensões na saída dos dois opamps de entrada (lembre que a corrente entrando na porta dos opamps é nula para chegar nas equações). Depois basta usar a configuração subtratora do opamp final.


Outras fontes

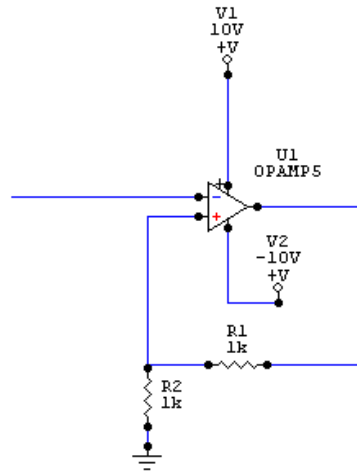

O1. Determine a saída em formato de gráfico v_{out} (eixo y) vs. V_{in} (eixo x) do circuito. Considere a entrada sendo aplicada no terminal inversor.

R: Curva histerese simétrica em torno do eixo v_{out} , com transições em $e_i = -5$ e 5

cap 17

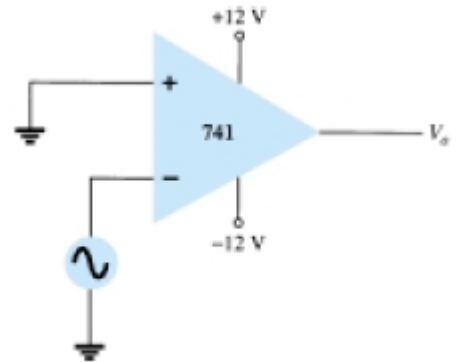

2. Sketch the output waveform for the circuit of Fig. 17.39.

Figure 17.39 Problem 2

R: onda quadrada oscilando entre 12 e -12, com polaridade invertida a senoide que é aplicada a entrada inversora