

**Lista 2 – Eletrônica Aplicada, Prof. Marcelo Perotoni**

*Capítulo 17 Boylestad, versão biblioteca UFABC em português*

17.1  $A_f = -9.95$


17.2 0.2%

17.3  $A_f = -14.3$     $Z_{if} = 31K5$     $Z_{of} = 2K4$

17.4 Atenção, erro na tradução brasileira, considere  $R_2 = 200K$        $A = -33.5$     $\beta = -0.2$     $A_f = -4.4$

17.5  $h_{ie} = 1.18K$     $Z_i = 1.18K$     $Z_o = R_C = 4K7$     $\beta = -R_E = -1200$     $A_f = -0.82E-3$     $A = -0.063$     $Z_{if} = 91.18K$   
 $Z_{of} = 363K$

*Exercício Prof. Hamilton Klimach, UFRGS, Eletrônica Fundamental*
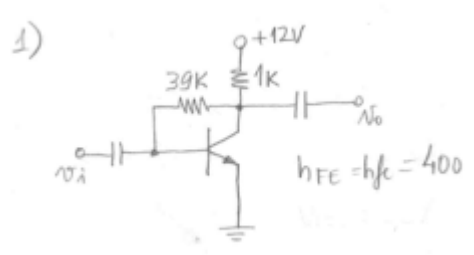
<p>(a) Calcule o ponto Q do transistor                  (b) Identifique o tipo de realimentação, tipo de amostra e comparação                  (c) Calcule o ganho A, <math>R_{if}</math> e <math>R_{of}</math>                  (d) Calcule <math>A_v</math> e <math>A_i</math></p> <p>Considere <math>h_{fe} = 400</math> e <math>V_{beq} = 0.6</math></p> <p><math>I_b = 2.57e-5</math>   <math>I_c = 10.3mA</math></p> <p>Amostra tensão, compara corrente, convenção Boylestad                  tensão em paralelo.</p> <p><math>h_{ie} = 1K</math>  <math>A = -(h_{fe}/h_{ie})[R_C/R_F][h_{ie}/R_F] = -380.25</math>  <math>\beta = -1/R_F = -2.56E-5</math>  <math>A_f = A/(1 + \beta A) = -377</math>  <math>Z_i = \text{resist entrada laço aberto} = 970</math>  <math>Z_o = \text{resist saída laço aberto} = 970</math>  <math>Z_{if} = \text{resist entrada realimentada} = 961</math>  <math>Z_{of} = \text{resist saída realimentada} = 961</math></p>	 <p>Hand-drawn circuit diagram of a common-emitter amplifier with feedback. The circuit includes a 39K resistor in the collector, a 1K resistor in the emitter, and a feedback resistor connected between the collector and emitter. The input is connected to the base through a coupling capacitor, and the output is taken from the collector through another coupling capacitor. A +12V supply is connected to the collector resistor. The transistor's beta is given as <math>h_{FE} = h_{fe} = 400</math>.</p>
---	--


*Capítulo 8 Sedra-Smith, versão original americana, 5ª edição*

**P\*8.35** Figure P8.35 shows a series–shunt feedback amplifier without details of the bias circuit.

- (a) Sketch the  $A$  circuit and the circuit for determining  $\beta$ .  
 (b) Show that if  $A\beta$  is large then the closed-loop voltage gain is given approximately by

$$A_f = \frac{V_o}{V_i} = \frac{R_F + R_E}{R_E}$$

- (c) If  $R_E$  is selected equal to 50  $\Omega$ , find  $R_F$  that will result in a closed-loop gain of approximately 25 V/V.  
 (d) If  $Q_1$  is biased at 1 mA,  $Q_2$  at 2 mA, and  $Q_3$  at 5 mA, and assuming that the transistors have  $h_{fe} = 100$ , find approximate values for  $R_{C1}$  and  $R_{C2}$  to obtain gains from the stages of the  $A$  circuit as follows: a voltage gain of  $Q_1$  of about -10 and a voltage gain of  $Q_2$  of about -50.  
 (e) For your design, what is the closed-loop voltage gain realized?  
 (f) Calculate the input and output resistances of the closed-loop amplifier designed.

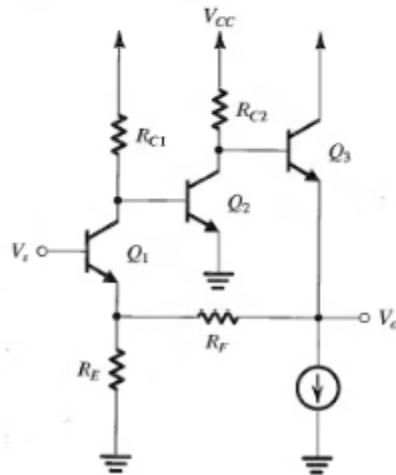

**FIGURE P8.35**

**8.36** For the circuit in Fig. 8.17(a), find an approximate value for  $I_o/V_s$  assuming that the loop gain is large. Use it to determine the voltage gain  $V_o/V_s$ . Compare your results with the values found in Example 8.2.

Amostra tensão, compara tensão, convenção Boylestad “tensão série”

- (a)  $\beta = R_E / (R_E + R_F)$   
 (b)  $A_f \approx 1 / \beta = 1 + (R_E / R_F)$   
 (c)  $R_F = 1200$   
 (d)  $r_{e1} = 26$   $r_{e2} = 13$   
 $r_{e3} = 5.2$   
 $A_{v1} = -10$   $A_{v2} = -50$   
 $R_{C1} = 1720$   $R_{C2} = 654$   
 $A_{v3} = 0.996$   
 (e)  $A = 498$   $A \beta = 19.92$   
 $e A_f = 23.8$   
 (f)  $R_i = 7K4$   $R_{if} = 154k$   
 $R_o = R_E / r_e = 11.12$   
 $R_{of} = 0.53$

Amostra corrente, compara tensão, convenção Boylestad “corrente série”

$$\beta = \frac{R_{E1} R_{E2}}{R_{E1} + R_{E2} + R_F} = 11.9$$

$$A_f^* = 1 / \beta = 84 \mu A/V$$

$$V_o / V_s = R_{C3} A_f^* = -50.4$$

