

1

The circuit of Fig. 9-17 is an *adjustable-output voltage regulator*. Assume that the basic op amp is ideal. Regulation of the Zener is preserved if $i_Z \geq 0.1I_Z$ (Section 2.10). (a) Find the regulated output v_o in terms of V_Z . (b) Given a specific Zener diode and the values of R_S and R_1 , over what range of V_S would there be no loss of regulation?

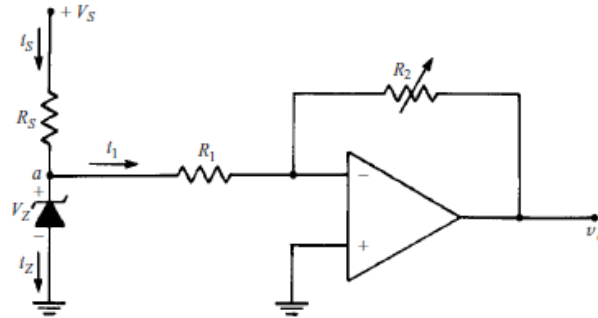


Fig. 9-17

$$v_o = -\frac{R_2}{R_1} V_Z$$

Respostas:

$$0.1I_Z R_S + \left(1 + \frac{R_S}{R_1}\right) V_Z \leq V_S \leq I_Z R_S + \left(1 + \frac{R_S}{R_1}\right) V_Z$$

9.8 In analog signal processing, the need often arises to introduce a *level clamp* (linear amplification to a desired output level or value and then no further increase in output level as the input continues to increase). One level-clamp circuit, shown in Fig. 9-16(a), uses series Zener diodes in a negative feedback path. Assuming ideal Zeners and op amp, find the relationship between v_o and v_S . Sketch the results on a transfer characteristic.


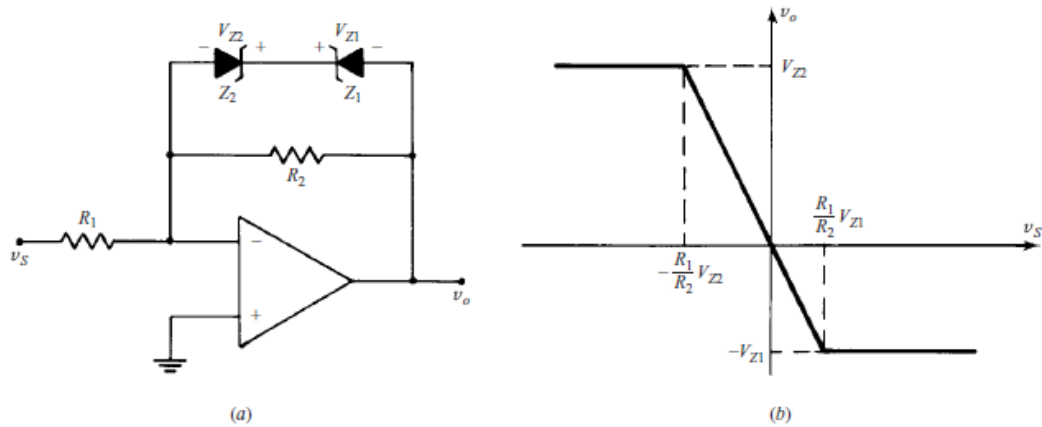


Fig. 9-16


Resultados: grafico acima (b)

$$v_o = \begin{cases} V_{Z2} & \text{for } v_S < -\frac{R_1}{R_2} V_{Z2} \\ -\frac{R_2}{R_1} v_S & \text{for } -\frac{R_1}{R_2} V_{Z2} \leq v_S \leq \frac{R_1}{R_2} V_{Z1} \\ -V_{Z1} & \text{for } v_S > \frac{R_1}{R_2} V_{Z1} \end{cases}$$

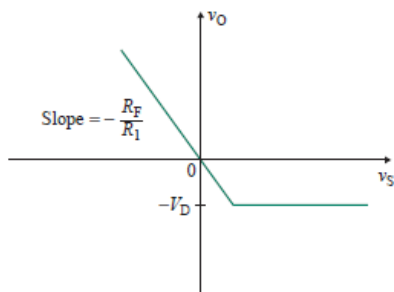3. No circuito ao lado esboce a curva (v_o) x (v_S).



R.

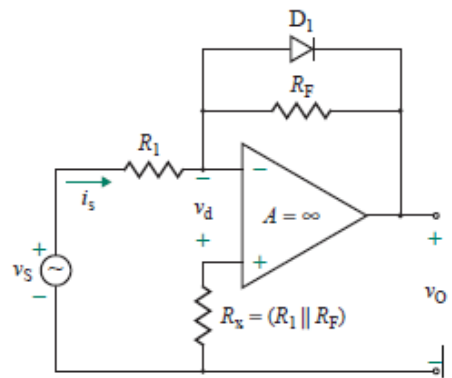

[5.11] Find v_o and i_o in the circuit in Figure 5.5.

R. $V_o = -2 \text{ V}$ e $i_o = -1 \text{ mA}$

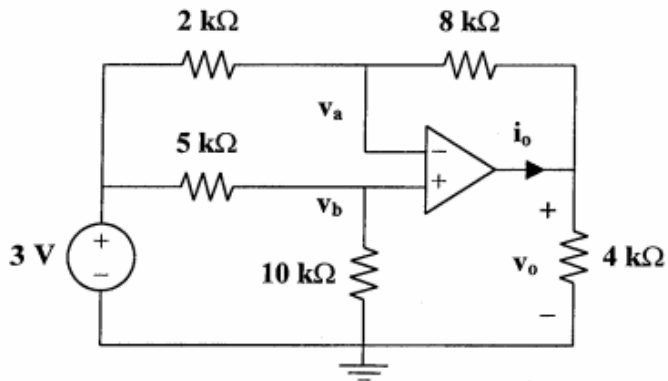


Figure 5.5

4.

5.

R. $V_o = -1.63 \text{ V}$

[5.19] Using the circuit in Figure 5.6, calculate v_o if $v_s = 0$.


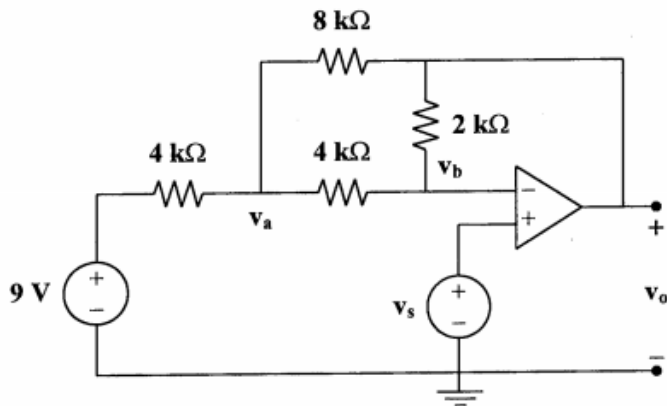



Figure 5.6

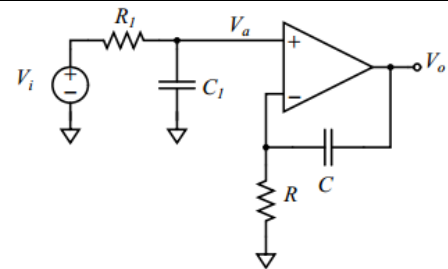6. Calcule o ganho em tensão do circuito. DICA – Use Laplace para representar os capacitores ($1/sC$)

R.
$$\frac{V_o(s)}{V_i(s)} = \frac{1}{R_1 C_1 s + 1} \frac{RCs + 1}{RCs}$$



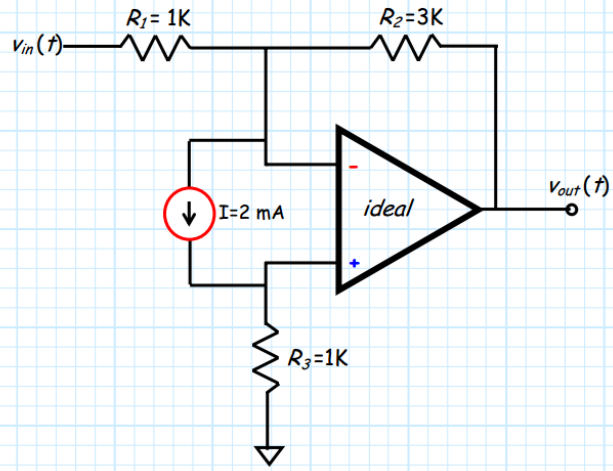Let's determine the output voltage $v_{out}(t)$ of the circuit below:



7.

R. $V_{out} = 14 - 3v_{in}$