

Exercícios

1) Monte os circuitos equivalentes (com portas lógicas) correspondentes as expressões lógicas:

- a) $a \cdot (c + b)'$
- b) $(a + b + c) \cdot d$
- c) $(d + c)' \cdot (a + b)'$
- d) $(p + q \cdot r)' \cdot (p \cdot q + r)' + p' \cdot q'$
- e) $(a + b + c)' \cdot d$
- f) $(p + q \cdot r) + p' \cdot r'$
- g) $(d \cdot c) \cdot (a + b)$
- h) $a \cdot (c + b)' + (a \cdot b + c) + a' \cdot c'$
- i) $(p + q \cdot r) \cdot (p \cdot q + r) + p' \cdot q' \cdot r'$

2) Monte a expressão lógica equivalente aos circuitos:

